

Assignment No. 6

Title :- Parity Generator

Objective :- Learn Even / Odd parity Generator / Checker using logic gates

Problem statement :- Design & Implement Parity Generator using EX-OR

Hardware & software requirement :-

Digital Trainer kit, IC 7486 (EX-OR), IC 7404 (NOT), IC 74180, Patch cord, +5V Power Supply

Theory :-

In digital communication, the digital data is sent over the telephone lines using different binary codes.

During the transmission, because of noise signal 0 may become 1 or vice versa and wrong information may be received at destination.

That's why at the receiving end, Parity will be checked.

Parity :- A term used to specify the number of one's in digital world as odd or even.

Parity checker: At receiving end a logic circuit is used to check the parity of received information.

Even bit parity code :- The total number of ones in parity code word is even.

Odd bit parity code :- The total number of ones in parity code word is odd.

Limitations :-

- 1) The one bit parity code word can detect one bit error.
- 2) It cannot detect the location of error & hence error cannot be corrected.

A) Even Parity Generator.

Truth Table :-


INPUT			OUTPUT
B_2	B_1	B_0	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

2) K-map for reduced Boolean Expression of output

$B_2 \backslash B_1$		B_0			
		00	01	11	10
0		0	1	0	1
1		1	0	1	0

$$P = B_2 \oplus B_1 \oplus B_0$$

 3) Circuit Diagram :- Even parity generator



B) Odd Parity Generator


INPUT			OUTPUT
B_2	B_1	B_0	P
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

2) K-map for reduction of boolean expression

B_2	B_1, B_0			
	00	01	11	10
0	1	0	1	0
1	0	1	0	1

$$P = B_2 \oplus B_1 \oplus B_0$$

3) Circuit Diagram:-

 

Outcome:-

Thus, we studied Parity generator/checker and their working & limitations.

