



ASSIGNMENT No. 2

Assignment 2: Design and Implement Half Subtractor and Full Subtractor a) Using Basic gates b) Using Universal

Objective:

a) To understand concept of Half add subtractor and full subtractor.

Hardware requirement:-

IC 7486, IC 7432, IC 7408, IC 7400, General purpose board, DC power supply, etc.

Outcomes:-

To design combinational circuit using K-map and Boolean algebra.

Theory:

The simplest binary subtractor is called half Subtractor. It has two inputs & two outputs. One output is Difference & the others is borrowed. They are represented by 'D' & 'B'. When two inputs borrow have to be subtracted the number of three input and input combinations increases to eight, for this full subtractor is used.


Procedure :-

- i] Verify the gates.
- ii] Make connections as per circuit diagram.
- iii] Switch on Vcc and apply various combination of input according to the truth table.

Half subtractor :-

Input		Output	
A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Circuit Diagram :-

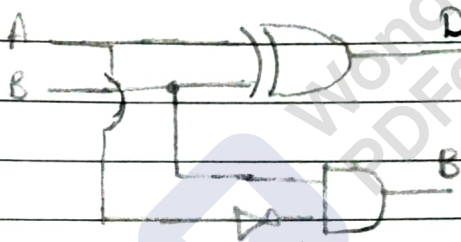


Truth Table :-


Input			Output	
A	B	B _{in}	D	B _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


Circuit Diagram :-

Using Basic Gates :-

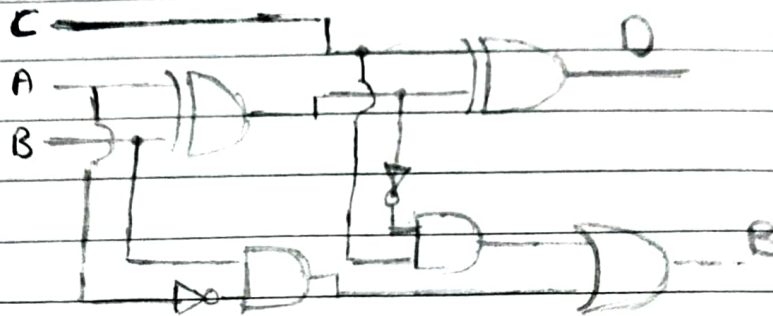

Using NAND gates :-

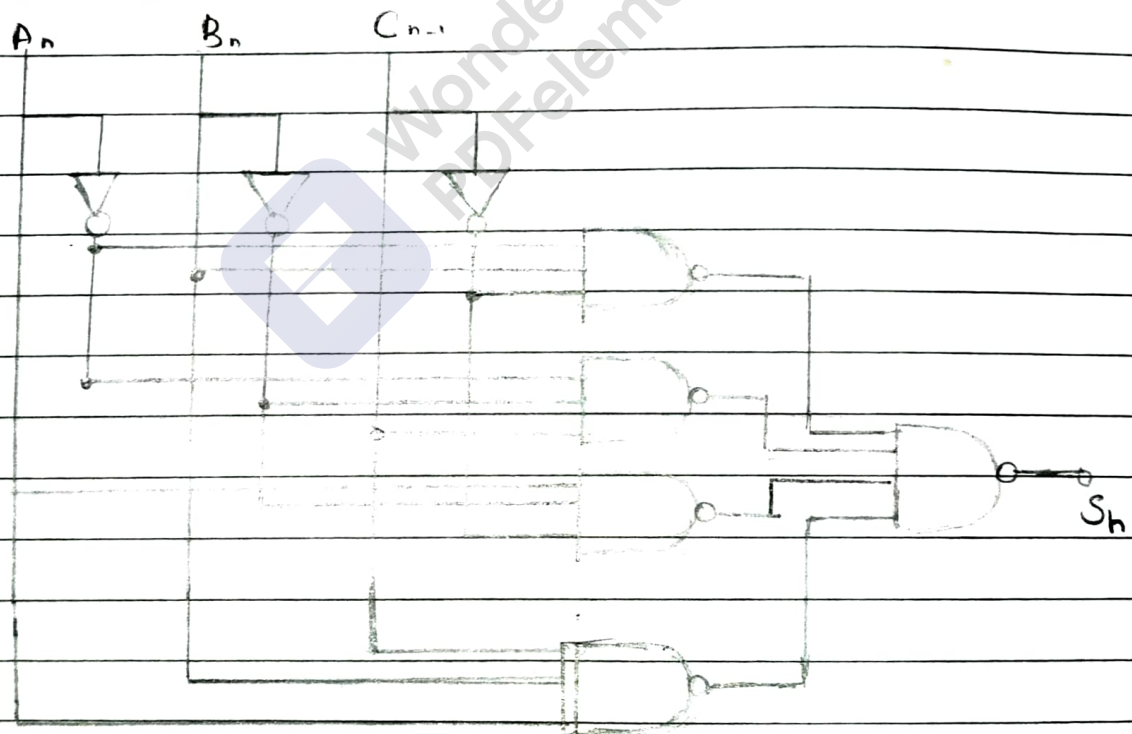

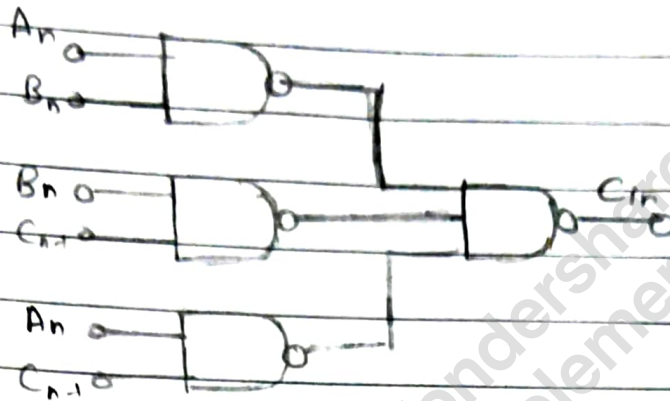

Conclusion :-

Thus realization of Half ^{subtractor}adder, full ^{subtractor}adder using basic gates & universal gates is done.

