

ASSIGNMENT NO. 4

Title :- BCD Adder

Objective :- To learn different types of adder

Problem statement :- Design and Realization of BCD Adder using 4-bit Binary Adder (IC 7483).

Hardware and Software requirements:-

Digital Trainer Kit, IC 7483, 7432, 7408, Patch cord, +5V Power Supply.

Theory :-

• BCD Adder :- It is a circuit that adds two BCD digits and produces a sum of digits also in BCD. BCD Numbers are 10 digits, 0 to 9 are represented in the binary form, i.e., each digit is represented as 4-bit binary number.

Rules for BCD Addition

1. Add two numbers using rules of Binary addition
2. If the 4-bit sum is greater than 9 or if carry is generated then the sum is invalid. To correct add 0110 to sum.
3. If the 4-bit sum is less than 9 or equal to 9 then sum is in proper form.

Case 1: sum ≤ 9 & carry = 0

Add BCD digit 3 & 4

$$\begin{array}{r} 0011 \\ + 0100 \\ \hline 0111 \end{array}$$

Answer is valid BCD.

Case II: Sum > 9 & carry $= 0$
Add BCD digits 6 & 5

$$\begin{array}{r} 0110 \\ + 0101 \\ \hline 1011 \end{array}$$

Invalid BCD as 0110 is added

$$\begin{array}{r} 1011 \\ + 0110 \\ \hline 10001 \end{array}$$

Valid BCD result = 11

Case III:

Sum < 9 & carry $\neq 0$
Add BCD digits 9 & 9

$$\begin{array}{r} 1001 \\ + 1001 \\ \hline 10010 \end{array}$$


Invalid BCD as 0110 is added

$$\begin{array}{r} 10010 \\ + 0110 \\ \hline 11000 \end{array}$$

Valid BCD result = 8

Design of BCD Adder:

 1. 4 bit binary adder is used for initial addition. i.e. Binary addition of two 4 bit numbers.
2. Logic circuit to sense if sum exceed 9 or carry = 1, this digital circuit will produce high output otherwise its output will be 0.
3. One more 4-bit adder to add (0110) 2 in the sum is greater than 9 or carry is 1.



Truth table for BCD Adder

Remove Watermark



Wondershare
PDFelement

INPUT				OUTPUT
S_3	S_2	S_1	S_0	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


Date _____
 Page _____

K-map :-

	$s_3 s_2$	$s_3 s_2$	00	01	11	10
00	0	0	0	0	0	0
01	0	0	0	0	0	0
11	1	1	1	1	1	1
10	0	0	1	1	1	1

$$Y = s_3 s_2 + s_3 s_1$$

Circuit Diagram:-

 



Observation table : of BCD Adder

INPUT								OUTPUT				
1 st Operand				2 nd Operand				MSD	LSD			
A ₃	A ₂	A ₁	A ₀	B ₃	B ₂	B ₁	B ₀	Carry	S ₃	S ₂	S ₁	S ₀
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	1	0	0	1	0	1	1	0	0	0	1
1	0	0	1	1	0	0	1	1	1	0	0	0

Outcomes :

Thus we studied single bit BCD adder using 4 bit parallel binary adder / 4 bit full adder. The observation table has been verified have been verified using IC 7483 & some logic gates.

